

# DC-AC Converter

B Swaroop Reddy and G V V Sharma\*

## CONTENTS

1	Components	1
2	Circuit Operation	1
3	Fourier Series Analysis of DC-AC Converter	2

**Abstract**—This manual provides the design of a DC-AC Converter.

## 1 COMPONENTS

Component	Value	Quantity
Arduino Uno		1
Capacitor	47 uF, 22 uF, 25 V	8 each
Capacitor	100 uF, 25 V	8
n-MOS	IRF 640	4
Jumper Wires	M-M	20
Diode	3 A	10
Gate Driver	TLP350	4
Transformers	12-0-12V, 3A	4

TABLE I

## 2 CIRCUIT OPERATION

The DC-AC converter Block diagram and circuit are shown in Fig. 1 and Fig. 2

**Problem 2.1.** Generate 4 dc sources of +12 V and -5 V each using the voltage regulator circuit as shown in the Fig.3

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

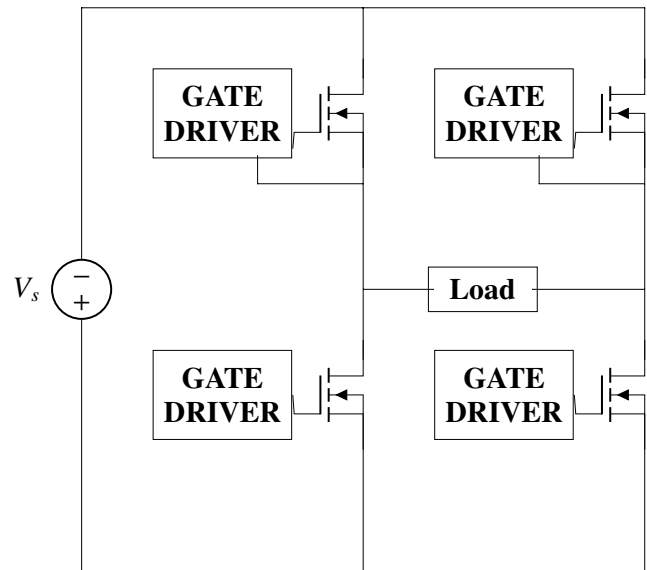


Fig. 1: DC-AC converter

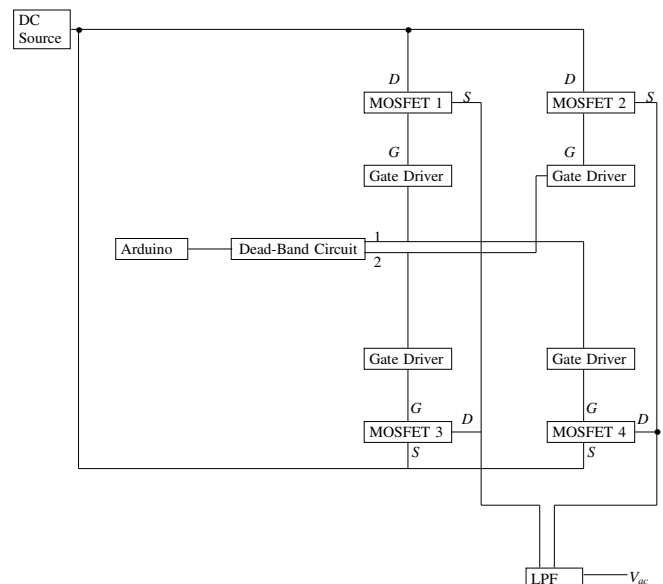


Fig. 2: DC-AC converter Block-diagram

**Problem 2.2.** Program the arduino to generate a square wave with *Duty Cycle*  $D = 0.5$  and frequency  $f = 50\text{Hz}$  and observe the waveform on the oscil-

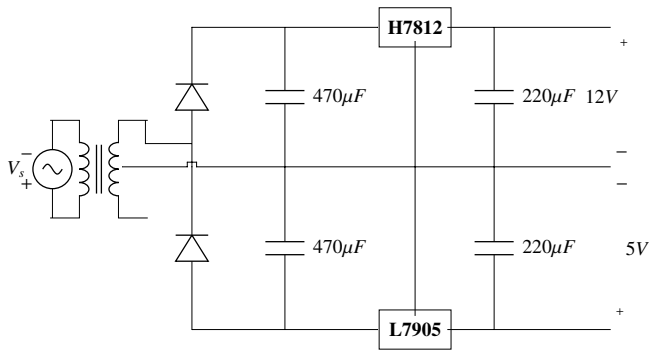


Fig. 3: Voltage-Regulator Circuit

loscope.

**Solution:**

```
void setup() {
  pinMode(13, OUTPUT);
}

void loop() {
  digitalWrite(13, LOW);
  delay(10);
  digitalWrite(13, HIGH);
  delay(10);
}
```

**Problem 2.3.** Calculate the R and C values for the dead band circuit shown in Fig.4 for the delay of 2.5 μsec.

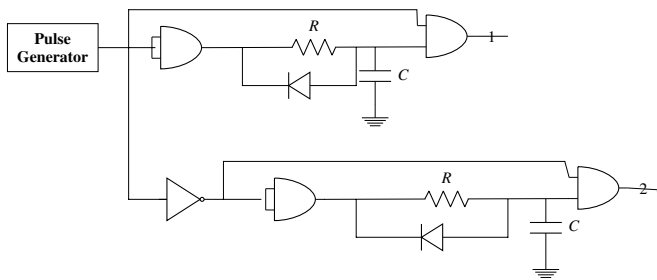


Fig. 4: Dead-Band Circuit

**Solution:**

$$V_{th}(\text{LogicGate}) = V_{pulse}(\text{Highlevel}) \times \left(1 - e^{-\frac{t}{RC}}\right)$$


$$RC = 3.82 \times 10^{-6}$$

selected R = 390Ω and C = 10nF

**Problem 2.4.** Connect the 13<sup>th</sup> pin of arduino to the Dead-band circuit and generate the Non-inverted(at 1) and Inverted(at 2) pulses and observe them on the oscilloscope.

**Problem 2.5.** Assemble the DC-AC circuit according to Figs. 1,2, 5 and Table II.

## Pin Configuration

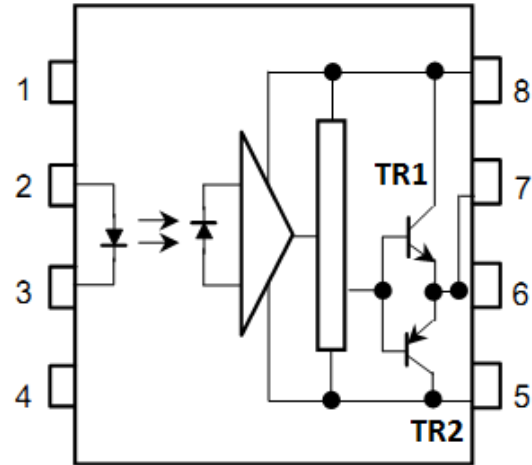

- 1 : N.C.
- 2 : Anode
- 3 : Cathode
- 4 : N.C.
- 5 : GND
- 6 : V<sub>O</sub> (Output)
- 7 : V<sub>O</sub>
- 8 : V<sub>CC</sub>

Fig. 5: TLP350

TLP350	1	2	3	4	5	6	7	8
ARDUINO	NA	13	GND	NA			NA	
					-5 V	10 Ω		12 V
MOSFET					S	G		

TABLE II: Pin Connections

## 3 FOURIER SERIES ANALYSIS OF DC-AC CONVERTER

**Problem 3.1.** Observe the output across the load in Fig. 1 on the oscilloscope. What do you observe?

**Problem 3.2.** Find the Fourier series expansion for the result in Problem.3.1.

**Problem 3.3.** Design a 4<sup>th</sup> order RC Low pass filter with cut-off frequency 50 Hz and observe the output of the Low pass filter.

**Problem 3.4.** Find the output of the lowpass filter designed in 3.3 with input as obtained from the result of 3.1. What do you observe?

**Problem 3.5.** Demonstrate your results through a Python script.