

POWER ELECTRONICS LABORATORY REPORT

Note:

Before going for connections, please read the datasheet of components used in the circuit.


Contents:	Pg.No.
1. Voltage Regulating Circuit	3
i) Aim	
ii) Circuit diagram	
iii) Components	
iv) Results	
2. Dead band circuit & Gate driver circuit	5
i) Aim	
ii) Circuit diagram	
iii) Formulas & Calculations	
iv) Components	
v) Results	
3. Half-bridge Inverter circuit	8
i) Aim	
ii) Circuit diagram	
iii) Formulas & Calculations	
iv) Components	
v) Results	
4. Full-bridge Inverter	10
i) Aim	
ii) Circuit diagram	
iii) Formulas & Calculations	
iv) Components	
v) Results	
5. Buck-Converter	12
i) Aim	
ii) Circuit diagram	
iii) Formulas & Calculations	
iv) Components	
v) Results	
6. Boost-Converter	15
i) Aim	
ii) Circuit diagram	
iii) Formulas & calculations	
iv) Components	
v) Results	

Experiment-1

Voltage Regulation Circuit

i) **Aim:** To generate regulated voltage levels of '**12V**' and '**-5V**' in order to provide as gate triggering levels for MOSFET in switching application.

ii) **Circuit diagram:**

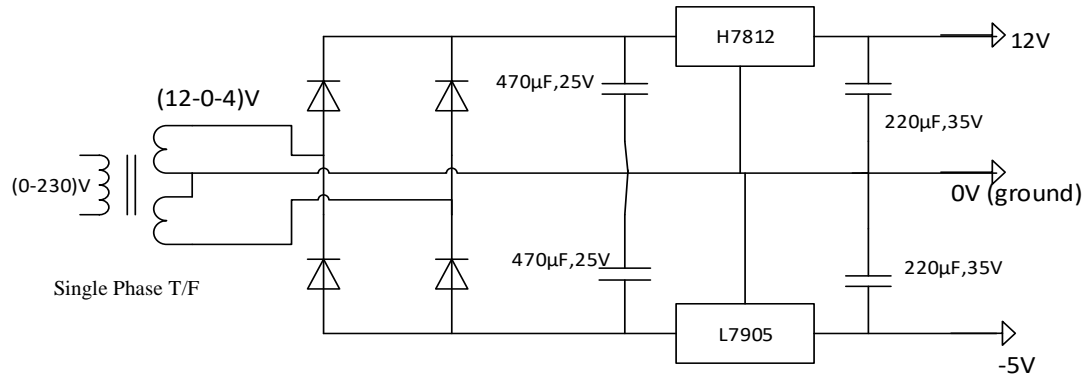


iii) **Components:**


S.No.	Component name	Rating	Quantity
1.	Capacitor	470 μ F, 25V	2
2.	Capacitor	220 μ F, 35V	2
3.	PN-junction diode	IN 4007	4
4.	Single phase transformer	(0-230)/(12-0-4)	1
5.	Positive voltage regulator	IC H7812	1
6.	Negative voltage regulator	IC L7905	1

iv) **Results:**

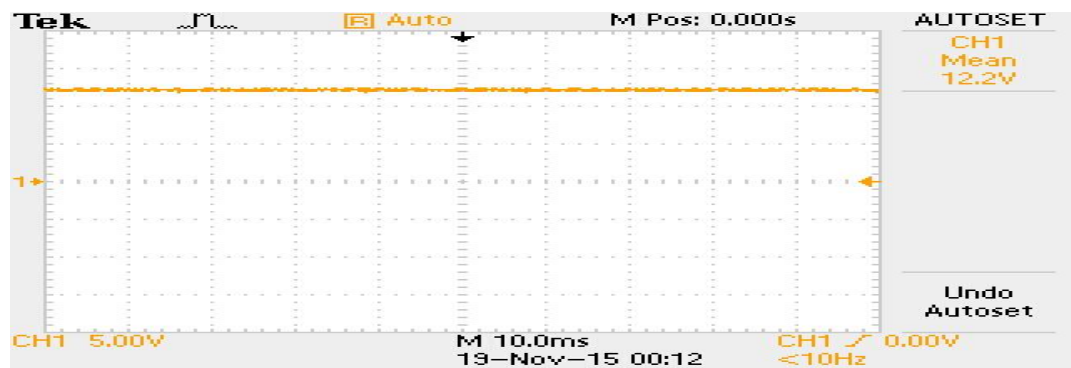a) Voltage waveform observed between the output terminal of IC H7812 (Positive voltage regulator) and ground terminal of Single phase transformer is



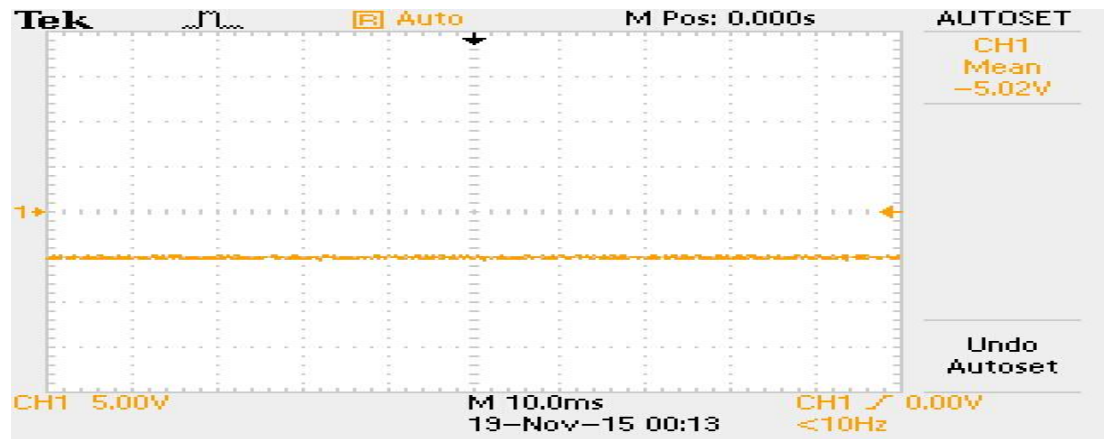- b) Voltage waveform observed between the output terminal of IC 7905 (Negative voltage regulator) and ground terminal of Single phase transformer is as




Experiment-2

Dead band circuit and Gate Driver Circuit


i) **Aim:** To design the Dead band circuit and Gate driver circuit for MOSFET.

ii) **Circuit diagram:**

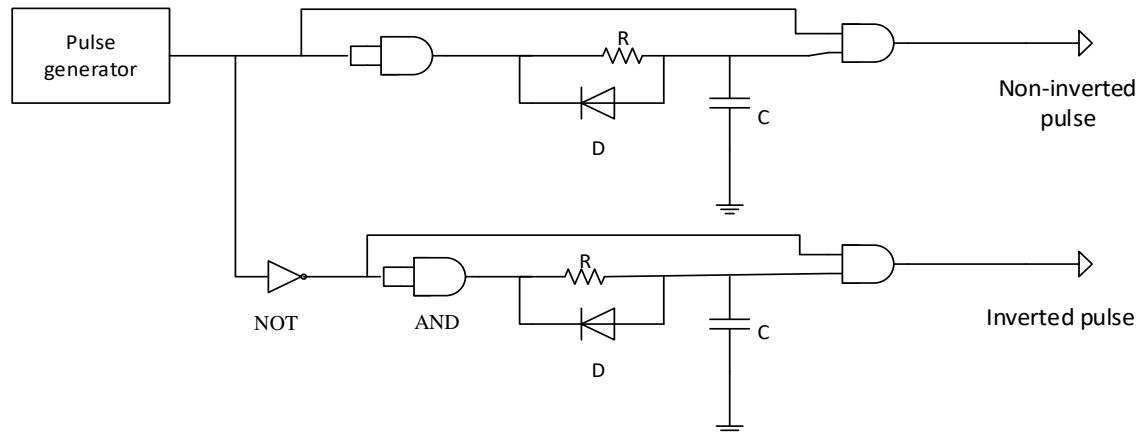a) **Dead band circuit:** To provide delay in generated pulses of gate driver circuit.



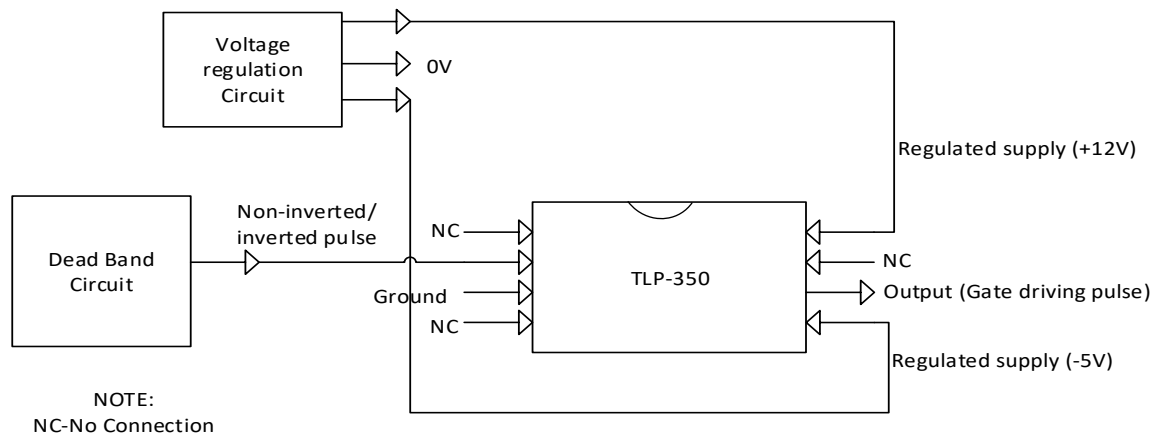b) **Gate Driver Circuit:** Generates pulse to drive MOSFET



iii) **Formulas & Calculations:**

$$V_{th}(\text{Logic gate}) = V_{\text{pulse}}(\text{High level}) \times (1 - e^{-t/RC})$$

$$\text{Let } t_{\text{delay}} = 2.50 \mu\text{s (typical value)} \rightarrow RC = 3.82 \times 10^{-6}$$


$$\text{Selected } R = 390 \Omega \text{ and } C = 10\text{nF}$$

iv) **Components:**


S.No.	Component	Rating	Quantity
1.	AND gate	IC 7408	1
2.	NOT gate	IC 7404	1
3.	Resistor	380 Ω	2
4.	Capacitor	10 nF, 100 V	2
5.	PN junction diode	IN 4007	2
6.	Gate driver	TLP 350	1
7.	Pulse generator		1

v) **Results:**a) *Dead band circuit:*

During OFF time

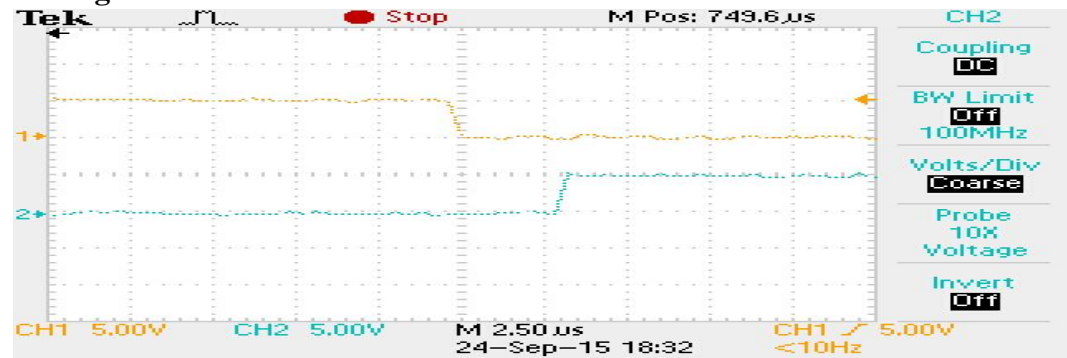
Off-time dead band observed = 2.50 μ s (approximately)

During ON time

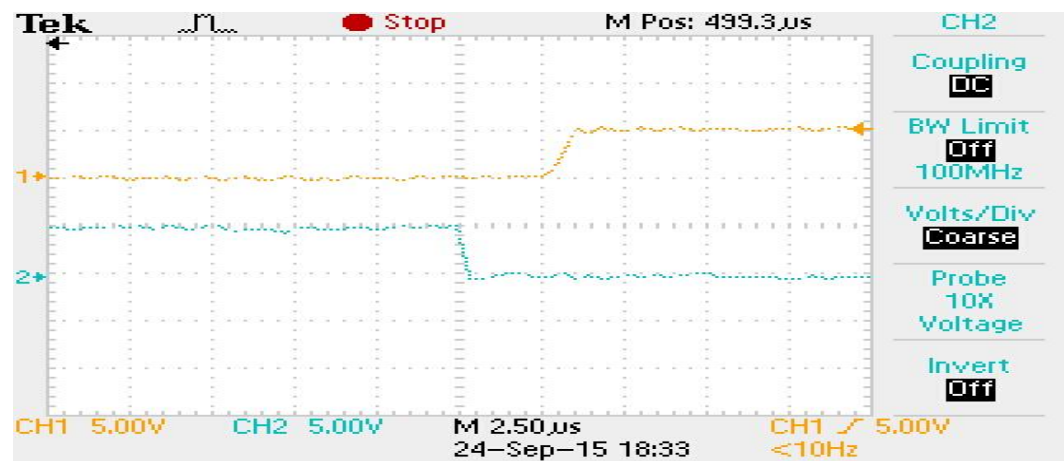On-time dead band = 2.50 μ s (approximately)

b) Gate driver circuit

Dead band during OFF time

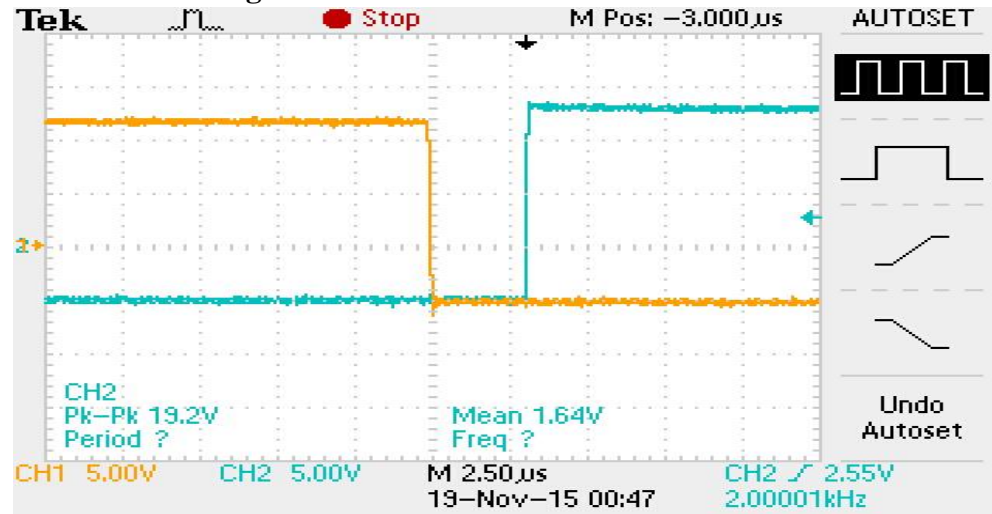


Pulse's high level = +12V

Pulse's low level = -5V

Off-time dead band for gate driving pulse = 2.50µs

Dead band during ON time

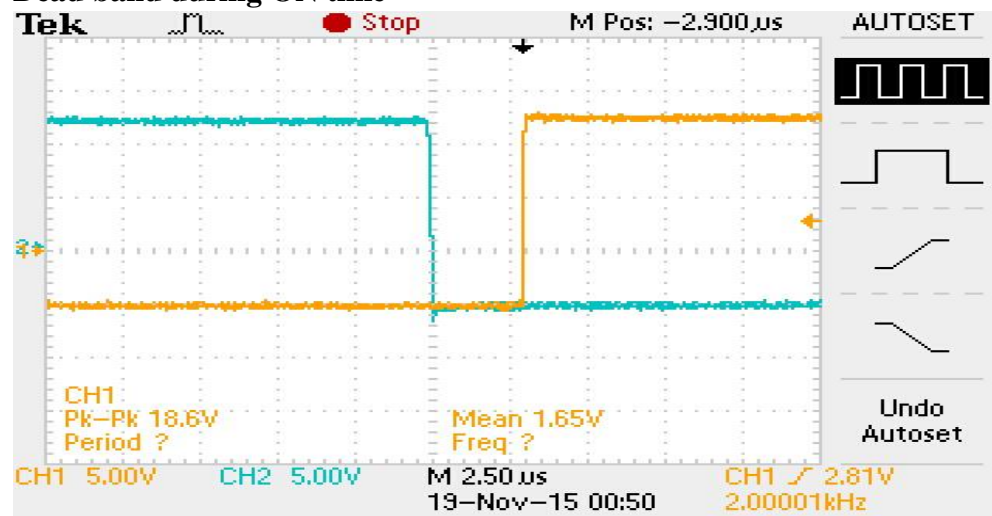

Pulse's high level = +12V (approx.)

Pulse's low level = -5V (approx.)


On-time dead band of gate driving pulse = 2.50µs (approx.)

Experiment-3

Single Phase Half-Bridge Inverter

i) **Aim:** To design a Single phase half-bridge inverter circuit using MOSFETs as switches.

ii) **Circuit diagram:**

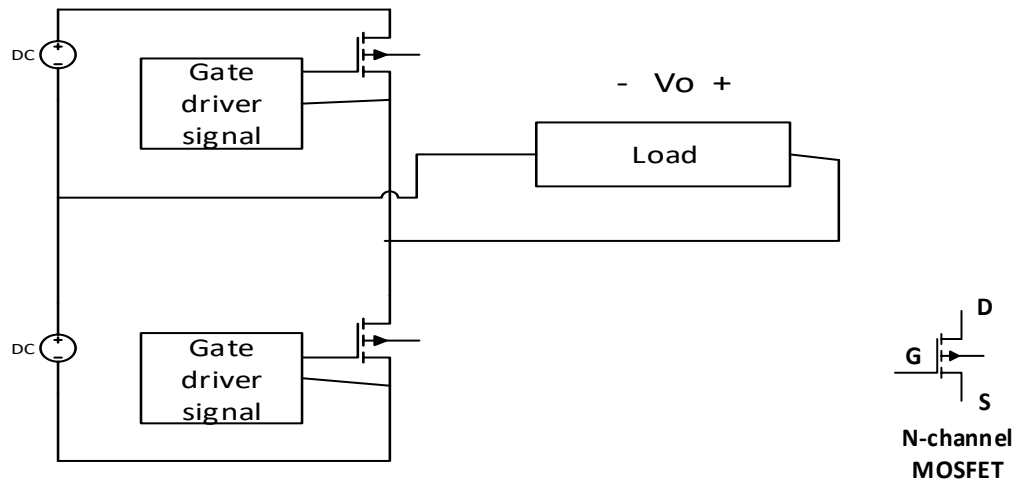


iii) **Components datasheet:**

S.No.	Component	Rating	Quantity
1.	MOSFET	IRF 740	2
2.	Rheostat	(0-220) Ω /2.8A	1
3.	Regulated DC supply	± 15 V, 3 A	1

iv) **Results:** $V_{DC} = 15$ V (approx.)

a) For frequency = 50 Hz

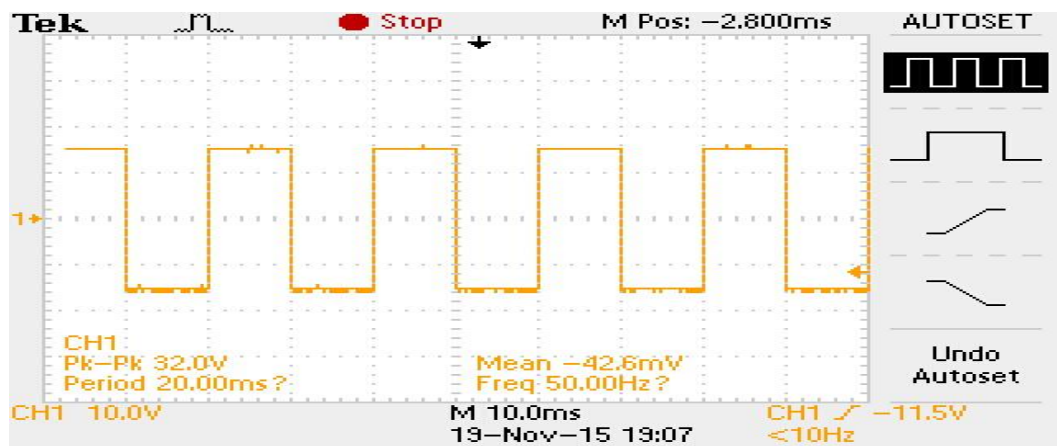

Peak- peak value of above waveform = 32V (approx.)

b) For frequency = 2 kHz




Peak-peak value of above waveform = 32 V (approx.)

Experiment-4

Single Phase Full Bridge Inverter

i) **Aim:** To design a Full-bridge inverter circuit using MOSFETs as switches.

ii) **Circuit diagram:**

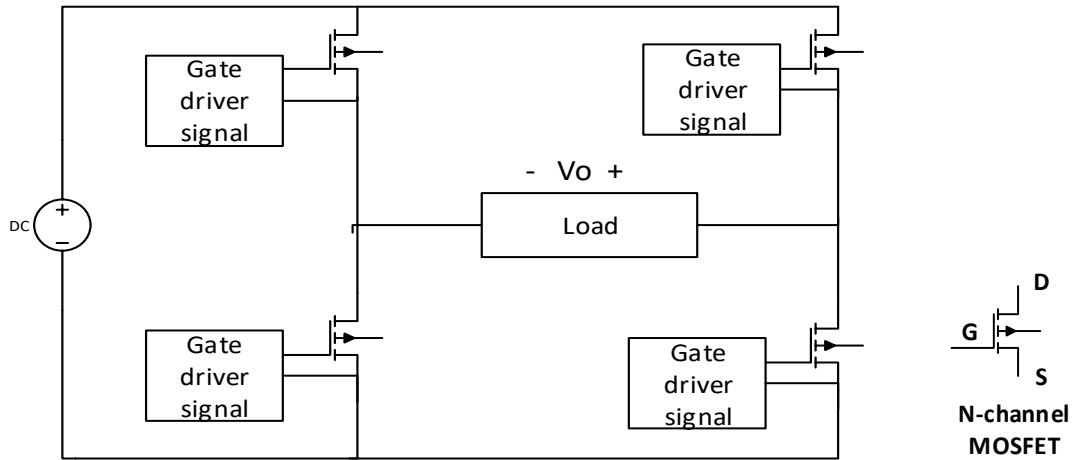


iii) **Components datasheet:**

S.No.	Component	Rating	Quantity
1.	MOSFET	IRF740	4
2.	Rheostat	(0-220) Ω /2.8A	1
3.	Inductor	2mH	1
4.	Regulated DC supply	± 15 V, 3 A	1


iv) **Output waveforms & Results:**

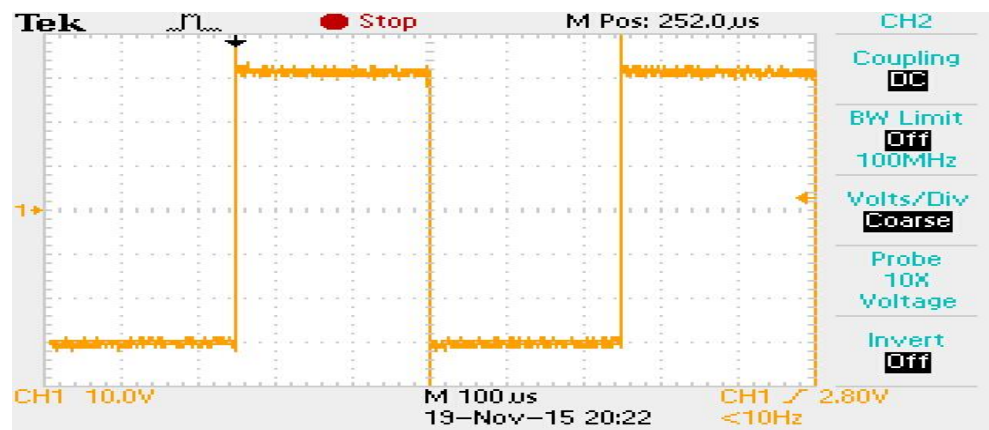a) Voltage between the pole points when there is no load



Positive peak = 30V (approx.); Negative peak = 30V (approx.) and frequency = 2 kHz

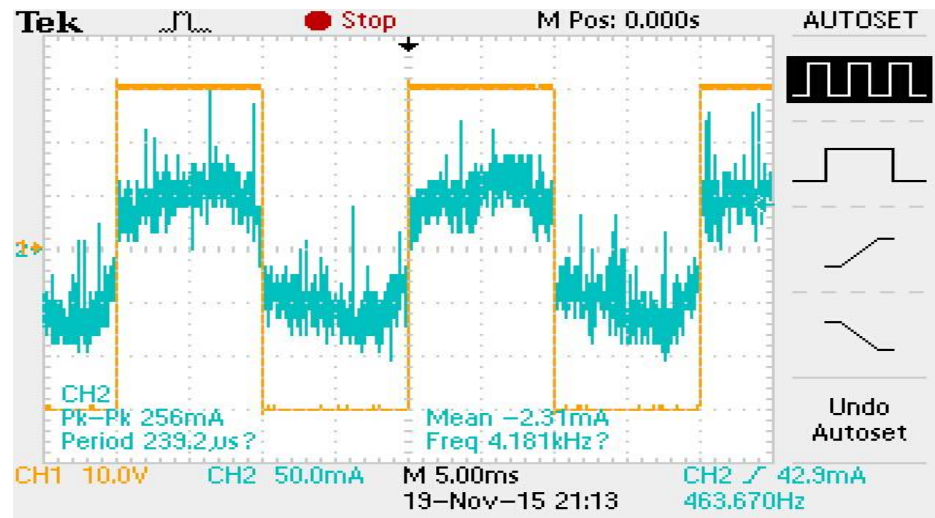b) When load is $R=220\Omega$ and $L=2\text{mH}$, The voltage across load and current through load



Voltage positive peak= 30V, negative peak = 30V and frequency =50Hz

Experiment-5

Buck Converter

- i) **Aim:** Designing of buck converter as per the specified requirements given below


Input voltage, $V_{in} = 15V$

Output voltage, $V_{out} = 6V$

Ripple current, $\Delta i_L = 11\%$ of I_{Load}

Ripple voltage, $\Delta V_{out} = 6\%$ of V_{out}

- ii) **Circuit diagram:**

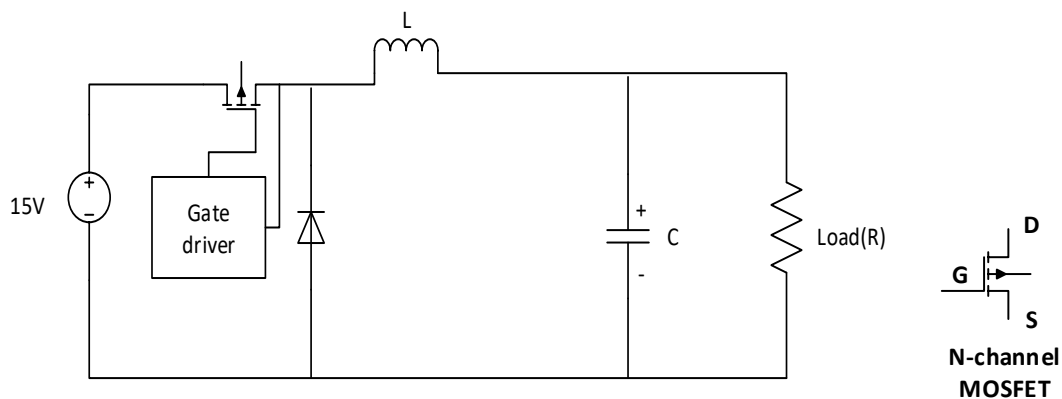

- iii) **Formulas & Calculations:**

$$L = \frac{V_{out}(1-D)}{\Delta i_L * f_s} \text{ H}$$

$$C = \frac{\Delta i_L}{8 * \Delta V_{out} * f_s} \text{ F}$$

$$D = \frac{V_{out}}{V_{in}}$$

Calculations:

Let $R_{Load} = 13 \Omega$; switching frequency $f_s = 36 \text{ kHz}$

$D = 0.4$

$I_{Load} = V_{out} / R_{Load} = 0.4615 \text{ A}$;

$\Delta i_L = 11\%$ of I_{Load} ;

$L = 2 \text{ mH}$;

$\Delta V_{out} = 0.36 \text{ V}$;

Selected $L = 2 \text{ mH}$; $C = (2.2 + 470) \mu\text{F}$

iv) **Components:**


S.No.	Component	Rating	Quantity
1.	MOSFET	IRF740	2
2.	Inductor	2mH	1
3.	Capacitor	472.2 μ F	1+1
4.	Rheostat	(0-220) Ω /2.8A	1
5.	Regulated DC supply	± 15 V, 3 A	1

v) **Results:**

a) Output voltage across load (rheostat)



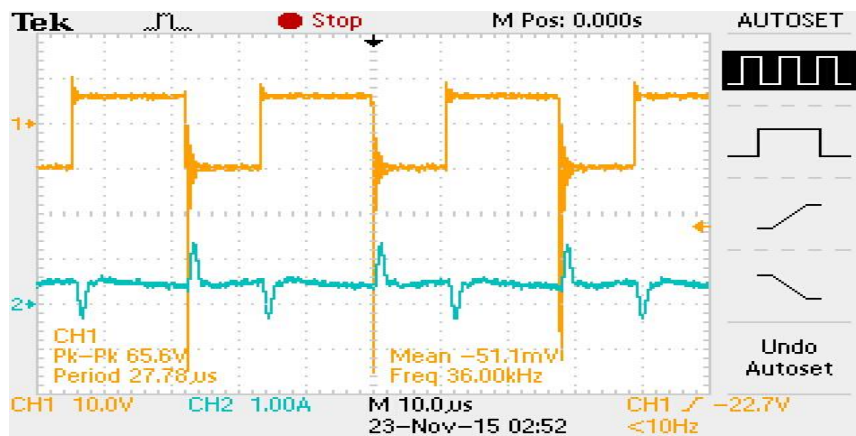b) Voltage across inductor and current through inductor waveforms



Observation: The surges in voltages waveforms during switching are due to values of Inductance and Capacitance present in the circuit.

c) Voltage across Inductor



Observation: The mean value of Voltage across Inductor over a period is observed as 40.3mV (Nearly zero) which represents the Voltage-sec balance and the deviation is due to disturbances.

Experiment-6

Boost Converter

- i) **Aim:** Designing of boost converter as per the specified requirements given below


Input voltage $V_{in} = 10\text{ V}$

Output Voltage $V_{out}=25\text{ V}$

%current ripple, $\Delta i_L = 5\%$ of I_{Load}

% voltage ripple, $\Delta V_{out} = 7\%$ of V_{out}

- i) **Circuit diagram:**

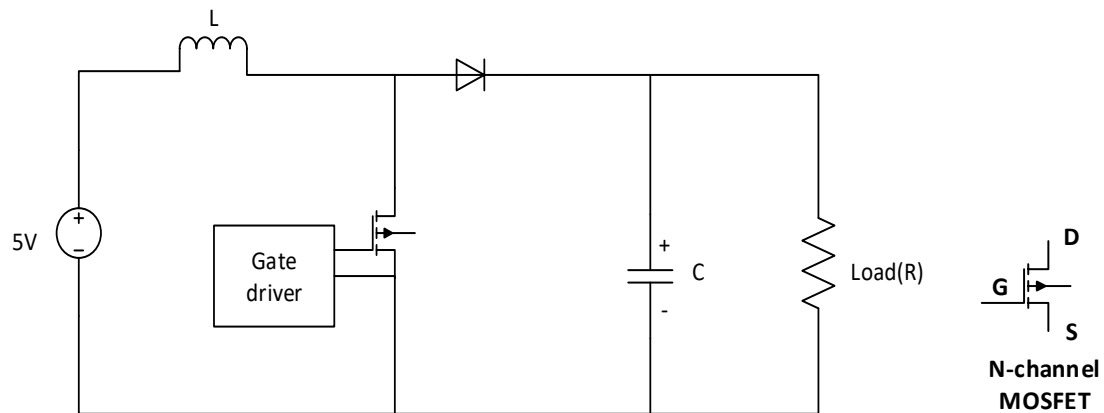

- ii) **Formulas & Calculations:**

$$\text{Duty ratio, } D = 1 - \frac{V_{in}}{V_{out}}$$

$$\text{Inductance, } L = V_{in} * \frac{D}{\Delta i_L * f_s}$$

$$\text{Capacitance, } C = I_{out} / (\Delta V_{out} * f_s)$$

Calculations:

$$\text{Let } R_{Load}=16\Omega;$$

$$V_{in}=10.4\text{ V};$$

$$D=60\%;$$



$$F_s=36\text{ kHz};$$

$$\text{Select } L=2\text{ mH}; C= (470+2.2)\mu\text{F}$$

$$\text{For selected } C, \Delta V_{out}=0.3\%$$

iii) **Components:**


S.No.	Component	Rating	Quantity
1.	MOSFET	IRF740	2
2.	Inductor	2mH	1
3.	Capacitor	$(470+2.2)\mu\text{F}$	1
4.	Rheostat	$220\Omega / 2.8\text{A}$	1
5.	Regulated DC supply	$\pm 15\text{ V}, 3\text{ A}$	1

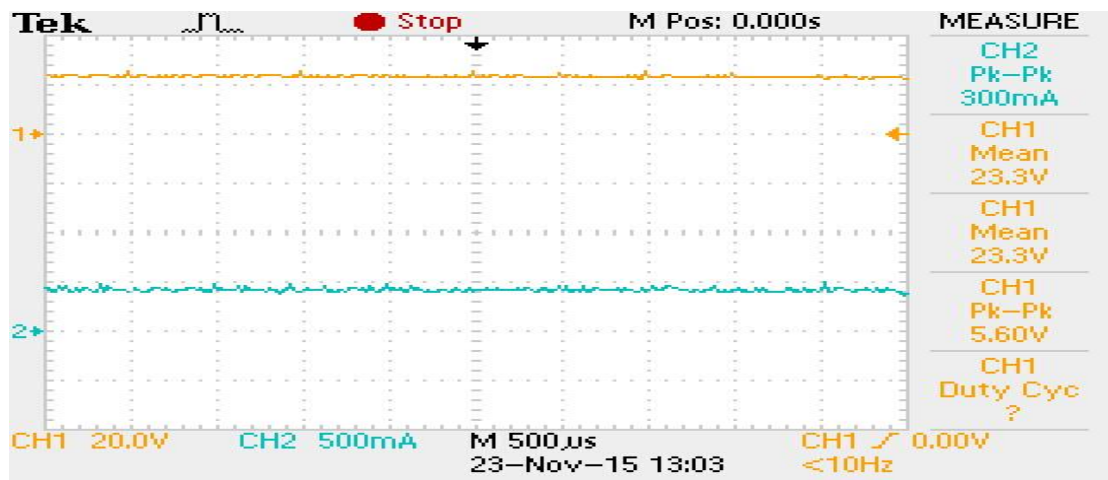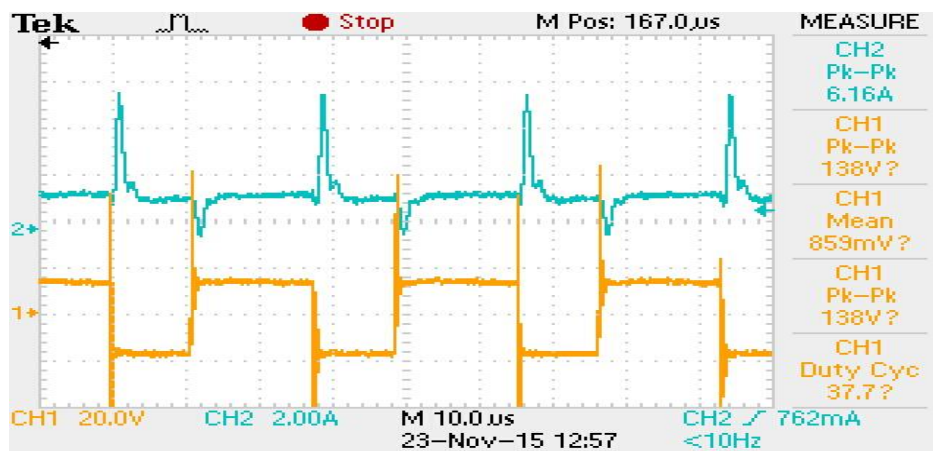iv) **Results:**a) *For Frequency, $f_s=36\text{kHz}$:***Voltage across load:**Voltage across load is observed as **23.3V**.**Current through Inductor and Voltage across inductor:**

Observation: From above waveform, Mean value of voltage across inductor over a period is **859mV** (which is close to zero), implies **volt-sec** balance across inductor over a period. This difference is mainly due to switching surges.


b) For Frequency, $f_s = 1 \text{ kHz}$:

Voltage across load:

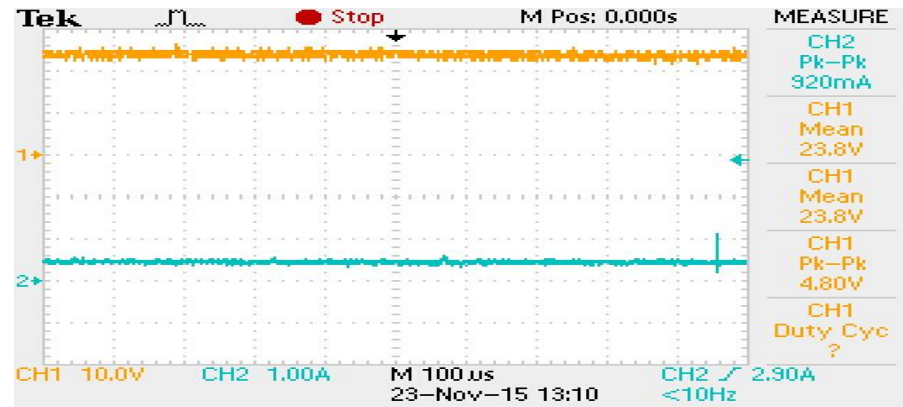

Observation: voltage across load=23.8V

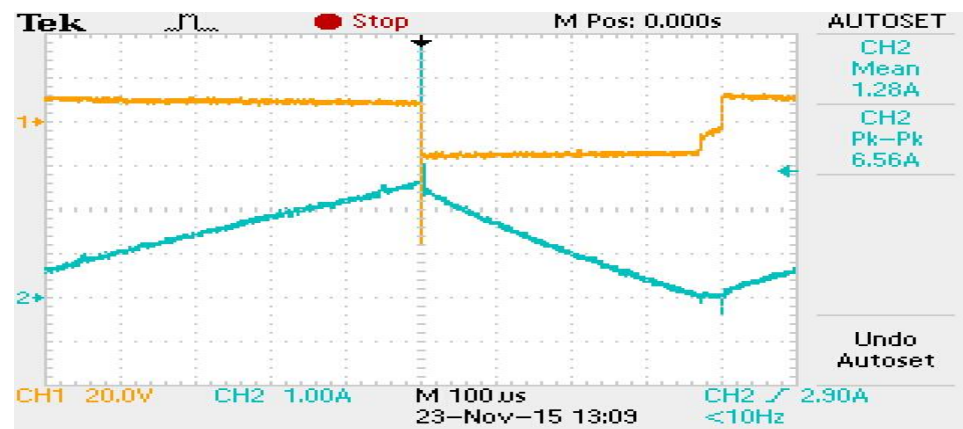Voltage across inductor and Current through Inductor:



Observations: We can observe the zero current through inductor for a short duration of time, representing the discontinuous mode of operation.