

B Swaroop Reddy and G V V Sharma\*

## CONTENTS

<b>1</b>	<b>Components</b>	<b>1</b>
<b>2</b>	<b>Circuit Diagram</b>	<b>1</b>
<b>3</b>	<b>Connections</b>	<b>1</b>
<b>4</b>	<b>Functioning</b>	<b>2</b>
4.1	Ripple Filter . . . . .	2
4.2	Regulator . . . . .	2
<b>5</b>	<b>Fourier series analysis of AC-DC converter</b>	<b>2</b>

**Abstract**—This manual provides the design of a mobile charger.

## 1 COMPONENTS

Component	Value	Quantity
Step Down Transformer	230V AC - 12V AC - 750 mA	1
Diode		4
Capacitor	100 $\mu$ F	1
Regulator	LM7805	1
Jumper Wires	M-M	20

TABLE I

## 2 CIRCUIT DIAGRAM

The circuit diagram is shown in 2.0

\*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

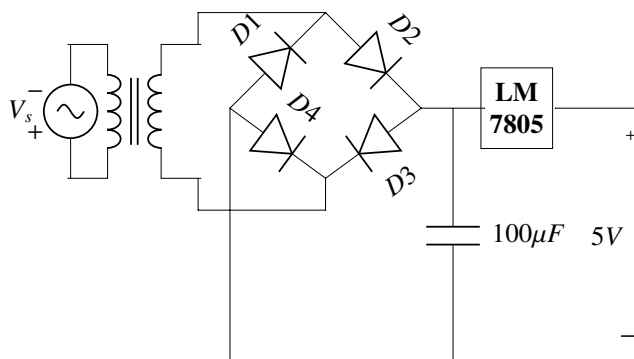


Fig. 2.0: AC-DC circuit diagram

## 3 CONNECTIONS

**Problem 3.1.** Connect the various components in Table I as per Fig. 2.0.

**Problem 3.2.** Observe the output of the Bridge Rectifier between junctions of D1,D4 and D2,D3 on oscilloscope. What do you observe?

**Solution:**

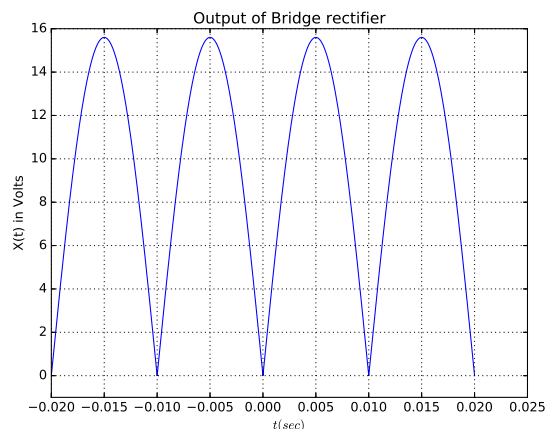


Fig. 3.2

## 4 FUNCTIONING

### 4.1 Ripple Filter

**Problem 4.1.** Measure the output of the capacitor filter using multimeter. What do you observe?

### 4.2 Regulator

The pin description of LM7805 is shown in Fig. 4.1

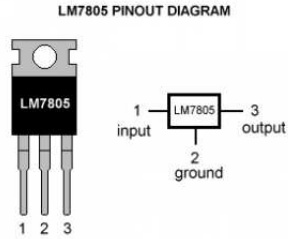


Fig. 4.1

**Problem 4.2.** Connect pin 1 and pin 2 of LM7805 to positive and Ground terminals of capacitor.

**Problem 4.3.** Measure the Voltage across and current passing through the pin 3 and Ground of LM7805. What do you observe?

## 5 FOURIER SERIES ANALYSIS OF AC-DC CONVERTER

**Problem 5.1.** The output of the transformer is 12V rms. Find the peak voltage from the rms voltage.

**Solution:**

$$V_m = \sqrt{2}V_{rms}$$

**Problem 5.2.** The threshold voltage for each diode in Fig. 2.0 is  $V_{th} = 0.7V$ . What is the peak voltage of the Bridge rectifier output?

**Solution:**

$$V_r = V_m - 2V_{th}$$

**Problem 5.3.** The Bridge rectifier output can be expressed as

$$V(t) = V_r |\sin(2\pi f_0 t)| \quad (5.3.1)$$

If

$$V(t) = \sum_{n=0}^{\infty} a_n \cos 2\pi n f_0 t + b_n \sin 2\pi n f_0 t \quad (5.3.2)$$

find  $a_n$  and  $b_n$ .

**Problem 5.4.** Assuming that  $f_0 = 100\text{Hz}$ , in Problem 5.3 compute  $a_0$  and compare it with the ripple filter output.

**Problem 5.5.** Demonstrate your results through a Python script.