

CONTENTS

| | | |
|---|--|---|
| 1 | Components | 1 |
| 2 | Circuit Operation | 1 |
| 3 | Fourier Series Analysis of DC-AC Converter | 2 |

Abstract—This manual provides the design of a DC-AC Converter.

1 COMPONENTS

| Component | Value | Quantity |
|--------------|--------------------|----------|
| Arduino Uno | | 1 |
| Capacitor | 47 uF, 22 uF, 25 V | 8 each |
| Capacitor | 100 uF, 25 V | 8 |
| n-MOS | IRF 640 | 4 |
| Jumper Wires | M-M | 20 |
| Diode | 3 A | 10 |
| Gate Driver | TLP350 | 4 |
| Transformers | 12-0-12V, 3A | 4 |

TABLE I

2 CIRCUIT OPERATION

The DC-AC converter Block diagram and circuit are shown in Fig. 1 and Fig. 2

Problem 2.1. Generate 4 dc sources of +12 V and -5 V each using the voltage regulator circuit as shown in the Fig.3

*The author is with the Department of Electrical Engineering, Indian Institute of Technology, Hyderabad 502285 India e-mail: gadepall@iith.ac.in. All content in this manual is released under GNU GPL. Free and open source.

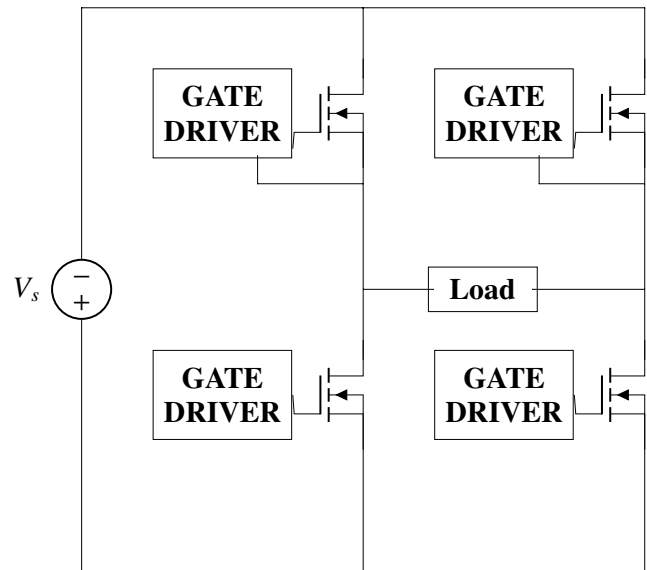


Fig. 1: DC-AC converter

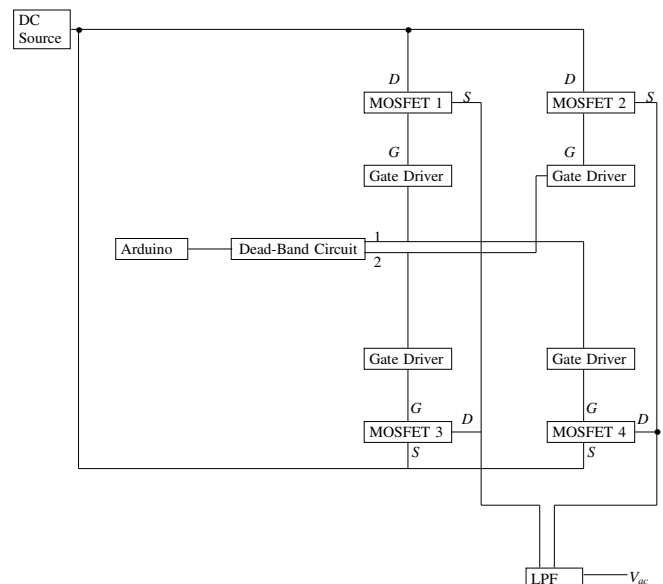


Fig. 2: DC-AC converter Block-diagram

Problem 2.2. Program the arduino to generate a square wave with *Duty Cycle* $D = 0.5$ and frequency $f = 50\text{Hz}$ and observe the waveform on the oscil-

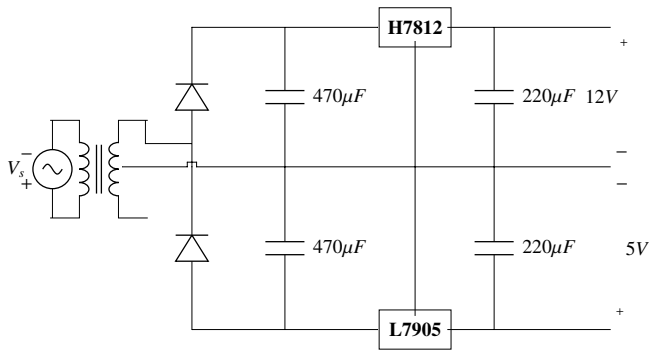


Fig. 3: Voltage-Regulator Circuit

loscope.

Solution:

```
void setup() {
  pinMode(13, OUTPUT);
}

void loop() {
  digitalWrite(13, LOW);
  delay(10);
  digitalWrite(13, HIGH);
  delay(10);
}
```

Problem 2.3. Calculate the R and C values for the dead band circuit shown in Fig.4 for the delay of 2.5 μsec.

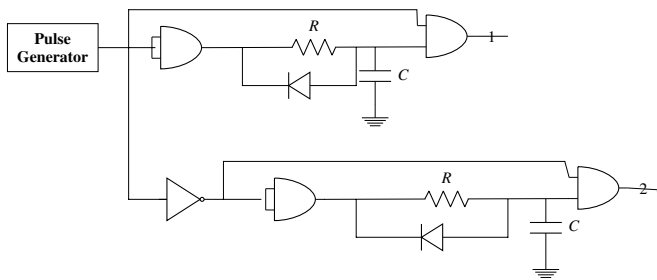


Fig. 4: Dead-Band Circuit

Solution:

$$V_{th}(\text{LogicGate}) = V_{pulse}(\text{Highlevel}) \times (1 - e^{-\frac{t}{RC}})$$


$$RC = 3.82 \times 10^{-6}$$

selected R = 390Ω and C = 10nF

Problem 2.4. Connect the 13th pin of arduino to the Dead-band circuit and generate the Non-inverted(at 1) and Inverted(at 2) pulses and observe them on the oscilloscope.

Problem 2.5. Assemble the DC-AC circuit according to Figs. 1,2, 5 and Table II.

Pin Configuration

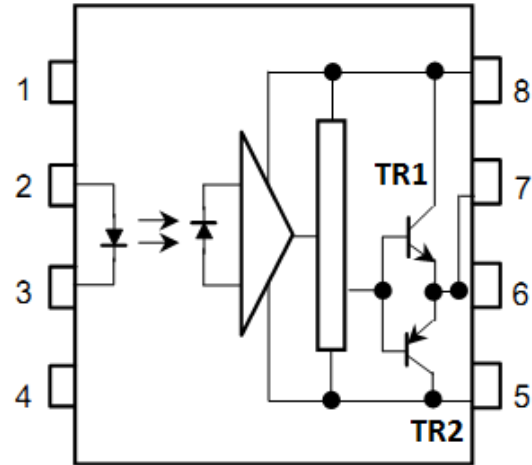

- 1 : N.C.
- 2 : Anode
- 3 : Cathode
- 4 : N.C.
- 5 : GND
- 6 : V_O (Output)
- 7 : V_O
- 8 : V_{CC}

Fig. 5: TLP350

| TLP350 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 |
|---------|----|----|-----|----|------|------|----|------|
| ARDUINO | NA | 13 | GND | NA | | | NA | |
| | | | | | -5 V | 10 Ω | | 12 V |
| MOSFET | | | | | S | G | | |

TABLE II: Pin Connections

3 FOURIER SERIES ANALYSIS OF DC-AC CONVERTER

Problem 3.1. Observe the output across the load in Fig. 1 on the oscilloscope. What do you observe?

Problem 3.2. Find the Fourier series expansion for the result in Problem.3.1.

Problem 3.3. Design a 4th order RC Low pass filter with cut-off frequency 50 Hz and observe the output of the Low pass filter.

Problem 3.4. Find the output of the lowpass filter designed in 3.3 with input as obtained from the result of 3.1. What do you observe?